

Résumé de dipôle RC : Charge

	Tension u_c	Charge q	Intensité i	Tension u_R
Equation différentielle	$RC \frac{du_c}{dt} + u_c = E$	$RC \frac{dq}{dt} + q = EC$	$RC \frac{di}{dt} + i = 0$	$RC \frac{du_R}{dt} + u_R = 0$
Solution de l'E.D.	$u_c(t) = E(1 - e^{-t/\tau})$	$q(t) = EC(1 - e^{-t/\tau})$	$i(t) = \frac{E}{R} e^{-t/\tau}$	$u_R(t) = E e^{-t/\tau}$
Conditions initiales $t = 0$	$u_c(0) = U_{c,0} = 0$	$q(0) = Q_0 = 0$	$i(0) = I_0 = \frac{E}{R}$	$u_R(0) = U_{R,0} = E$
Régime permanent $t \rightarrow \infty$	$u_c(\infty) = U_{c,max} = E$	$q(\infty) = Q_{max} = EC$	$i(\infty) = I_{max} = 0$	$u_R(\infty) = U_{R,max} = 0$
$t = \tau$	$u_c(\tau) = 0,63 \cdot E$	$q(\tau) = 0,63 \cdot EC$	$i(\tau) = 0,37 \cdot \frac{E}{R}$	$u_R(\tau) = 0,37 \cdot E$
Graphes				

Résumé de dipôle RC : Décharge

	Tension u_c	Charge q	Intensité i	Tension u_R
Equation différentielle	$RC \frac{du_c}{dt} + u_c = 0$	$RC \frac{dq}{dt} + q = 0$	$RC \frac{di}{dt} + i = 0$	$RC \frac{du_R}{dt} + u_R = 0$
Solution de l'E.D.	$u_c(t) = Ee^{-t/\tau}$	$q(t) = ECe^{-t/\tau}$	$i(t) = -\frac{E}{R}e^{-t/\tau}$	$u_R(t) = -Ee^{-t/\tau}$
Conditions initiales $t = 0$	$u_c(0) = U_{c,0} = E$	$q(0) = Q_0 = EC$	$i(0) = I_0 = -\frac{E}{R}$	$u_R(0) = U_{R,0} = -E$
Régime permanent $t \rightarrow \infty$	$u_c(\infty) = U_{c,max} = 0$	$q(\infty) = Q_{max} = 0$	$i(\infty) = I_{max} = 0$	$u_R(\infty) = U_{R,max} = 0$
$t = \tau$	$u_c(\tau) = 0,37 \cdot E$	$q(\tau) = 0,37 \cdot EC$	$i(\tau) = 0,37 \cdot \left(-\frac{E}{R}\right)$	$u_R(\tau) = 0,37 \cdot (-E)$
Graphes				